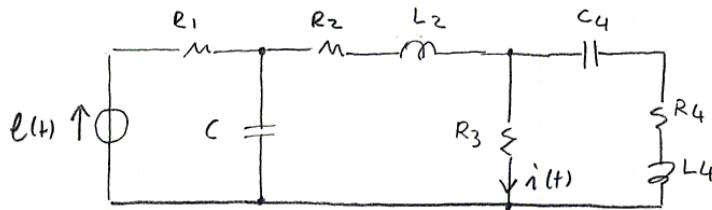


1) DETERMINARE $e(t)$ SAPENDO CHE $i(t) = 3 \cos(200t + 45^\circ) \text{ A}$




$$\begin{aligned} R_1 &= 10 \Omega & C &= 1 \text{ mF} \\ R_2 &= 5 \Omega & C_4 &= 2,5 \text{ mF} \\ R_3 &= 4 \Omega & L_2 &= 10 \text{ mH} \\ R_4 &= 8 \Omega & L_4 &= 25 \text{ mH} \end{aligned}$$

2) ESPRIMERE LE SEGUENTI SOMME DI SINUSOIDI NELLA FORMA $A \cos(\omega t + \phi)$

$$- v_1(t) = 3 \cos(2t + 60^\circ) + 8 \cos(2t - 22,5^\circ) \text{ V}$$

$$- v_2(t) = 2\sqrt{2} \sin 4t + 10 \cos(4t + 30^\circ) \text{ V}$$

3) DETERMINARE $v_o(t)$

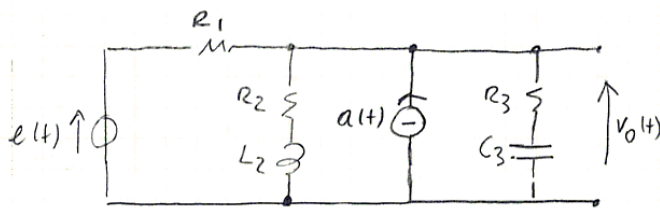

$$e(t) = 20 \cos(\omega_0 t + 90^\circ) \text{ V}$$

$$a(t) = 6 \cos \omega_0 t \text{ A}$$

$$\omega_0 = 10^5 \text{ rad/s} \quad L_2 = 30 \mu\text{H}$$


$$R_1 = 1 \Omega$$

$$R_3 = 3 \Omega$$

$$R_2 = 4 \Omega$$

$$C_3 = 2,5 \mu\text{F}$$

4) DETERMINARE $i(t)$

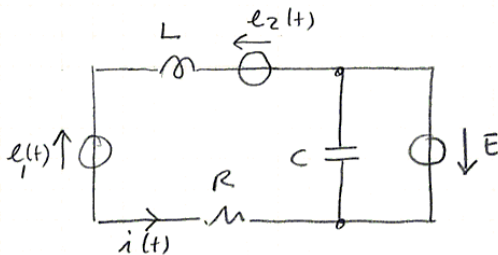

$$e_1(t) = 12 \cos(4000t + 45^\circ) \text{ V}$$

$$e_2(t) = 5 \sin 4000t \text{ V}$$

$$E = 3 \text{ V}$$

$$R = 3 \text{ k}\Omega$$

$$L = 50 \text{ mH}$$

$$C = 1 \mu\text{F}$$


1) ESPRIMERE LE SEGUENTI SORME DI SINUSOIDI NELLA FORMA GENERALE

$$A \sin(\omega t + \phi)$$

$$- i(t) = 2 \cos(6t + 120^\circ) + 4 \sin(6t - 60^\circ) \text{ A}$$


$$- v(t) = 5\sqrt{2} \cos 8t + 10 \sin(8t + 45^\circ) \text{ V}$$

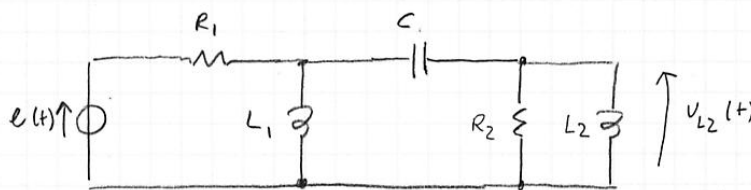2) DETERMINARE $e(t)$ SAPENDO CHE $v_{L2}(t) = 10 \cos 400t \text{ V}$




$$\begin{aligned} R_1 &= 25 \Omega \\ L_1 &= 0,06 \text{ H} \\ C &= 80 \mu\text{F} \\ R_2 &= 40 \Omega \\ L_2 &= 0,15 \text{ H} \end{aligned}$$

3) DETERMINARE $i(t)$

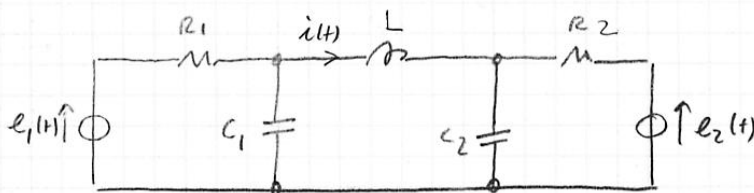

$$\begin{aligned} e_1(t) &= 10 \cos \omega t \text{ V} \\ e_2(t) &= 10 \sin \omega t \text{ V} \\ \omega &= 1000 \text{ rad/s} \\ R_1 &= 10 \Omega \quad R_2 = 1 \Omega \\ C_1 &= C_2 = 1 \text{ mF} \quad L = 1 \text{ mH} \end{aligned}$$

4) DETERMINARE $i(t)$

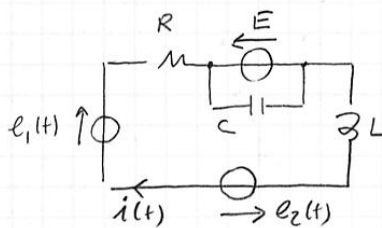

$$e_1(t) = 12 \cos(4t + 45^\circ) \text{ V}$$

$$e_2(t) = 5 \sin 4t \text{ V}$$


$$E = 3 \text{ V}$$

$$R = 6 \text{ k}\Omega$$

$$L = 0,5 \text{ H}$$

$$C = 100 \mu\text{F}$$

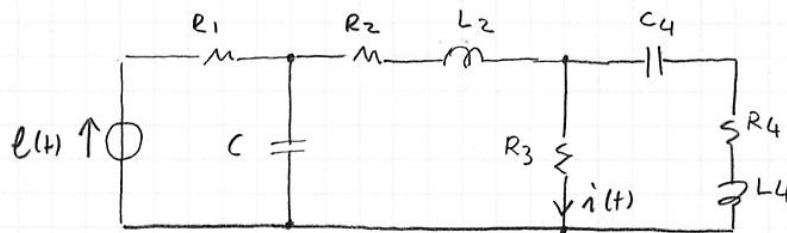1) DETERMINARE $e(t)$ SAPENDO CHE $i(t) = 3 \cos(200t + 45^\circ) \text{ A}$



$$\begin{aligned} R_1 &= 10 \Omega \\ R_2 &= 5 \Omega \\ R_3 &= 4 \Omega \\ R_4 &= 8 \Omega \end{aligned}$$

$$\begin{aligned} C &= 1 \text{ mF} \\ C_4 &= 2,5 \text{ mF} \\ L_2 &= 10 \text{ mH} \\ L_4 &= 25 \text{ mH} \end{aligned}$$

DATI	
$i(t) = 3 \cos(200t + 45^\circ) \text{ V}$	
ω	200
R_1	10
R_2	5
R_3	4
R_4	8
L_2	0,01
L_4	0,025
C	0,001
C_4	0,0025
FASORI E IMPEDENZE	
I	$2,12132034355964 + 2,12132034355964j$
Z_{L2}	$2j$
Z_{L4}	$5j$
Z_C	$-5j$
Z_{C4}	$-2j$
SOLUZIONE	
$V_3 = R_3 \cdot I$	$8,48528137423856 + 8,48528137423856j$
$Z_4 = R_4 + Z_{C4} + Z_{L4}$	$8 + 3j$
$I_4 = V_3 / Z_4$	$1,27860404269348 + 0,581183655769764j$
$I_2 = I + I_4$	$3,39992438625312 + 2,7025039993294j$
$Z_2 = R_2 + Z_{L2}$	$5 + 2j$
$V_2 = Z_2 \cdot I_2$	$11,5946139326068 + 20,3123687691532j$
$V_C = V_2 + V_3$	$20,0798953068454 + 28,7976501433918j$
$I_C = V_C / Z_C$	$-5,75953002867836 + 4,01597906136908j$
$I_1 = I_2 + I_C$	$-2,35960564242524 + 6,71848306069848j$
$V_1 = R_1 \cdot I_1$	$-23,5960564242524 + 67,1848306069848j$
$E = V_1 + V_C$	$-3,516161117407 + 95,9824807503766j$
$ E $	96,04686356
φ	92,09799895
$e(t) = 96,047 \cos(\omega t + 92,10^\circ) \text{ V}$	

2) ESPRIMERE LE SEGUENTI SOMME DI SINUSOIDI NELLA FORMA $A \cos(\omega t + \phi)$

$$- v_1(t) = 3 \cos(2t + 60^\circ) + 8 \cos(2t - 22,5^\circ) \text{ V}$$

$$- v_2(t) = 2\sqrt{2} \sin 4t + 10 \cos(4t + 30^\circ) \text{ V}$$

$$2) \quad v_1 = 3 \cos(2t + 60^\circ) + 8 \cos(2t - 22,5^\circ)$$

$$\bar{v}_1 = 3 e^{j60^\circ} + 8 e^{-j22,5^\circ} = v_1 e^{j\phi} = 8,9 \angle -2,98^\circ \text{ V}$$


$$v_1(t) = \mathcal{R}[\bar{v}_1 e^{j\omega t}] = v_1 \cos(2t + \phi) = 8,9 \cos(2t - 2,98^\circ) \text{ V}$$

$$v_2 = 2\sqrt{2} \sin 4t + 10 \cos(4t + 30^\circ)$$

$$\bar{v}_2 = -j2\sqrt{2} + 10 e^{j30^\circ} = v_2 e^{j\phi} = 8,93 \angle 14,08^\circ \text{ V}$$

$$v_2(t) = \mathcal{R}[\bar{v}_2 e^{j\omega t}] = v_2 \cos(4t + \phi) = 8,93 \cos(4t + 14,08^\circ) \text{ V}$$

3) DETERMINARE $V_0(t)$

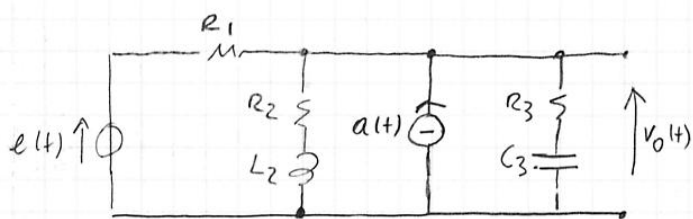

$$e(t) = 20 \cos(\omega_0 t + 90^\circ) \text{ V}$$

$$a(t) = 6 \cos \omega_0 t \text{ A}$$

$$\omega_0 = 10^5 \text{ rad/s}$$

$$L_2 = 30 \mu\text{H}$$

$$R_1 = 1 \Omega$$


$$R_3 = 3 \Omega$$

$$R_2 = 4 \Omega$$

$$C_3 = 2,5 \mu\text{F}$$

DATI	
$e(t)=20\cos(\omega t+90^\circ) \text{ V}$	
$a(t)=6\cos(\omega t) \text{ A}$	
ω	100000
R1	1
R2	4
R3	3
L2	0,00003
C3	0,0000025
FASORI E IMPEDENZE	
E	1,22514845490862E-15+20j
A	6
ZL2	3j
ZC3	-4j
SOLUZIONE	
$A_e=E/R_1$	1,22514845490862E-15+20j
$A_t=A_e+A$	6+20j
$Z_2=R_2+Z_{L2}$	4+3j
$Z_3=R_3+Z_{C3}$	3-4j
$Z_2//Z_3$	3,5-0,5j
$Z_P=R_1/(Z_2//Z_3)$	0,780487804878049-0,024390243902439j
$V_o=A_t*Z_P$	5,17073170731707+15,4634146341463j
$ V_o $	16,30501943
φ	71,51084516
$v_o(t)=16,305\cos(\omega t+71,51^\circ) \text{ V}$	

4) DETERMINE $i(t)$

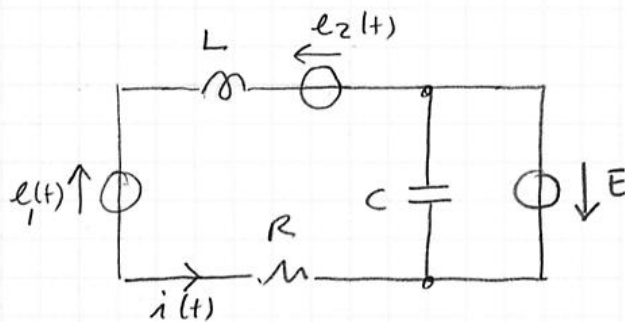

$$e_1(t) = 12 \cos(4000t + 45^\circ) \text{ V}$$

$$e_2(t) = 5 \sin 4000t \text{ V}$$


$$E = 3 \text{ V}$$

$$R = 3 \text{ k}\Omega$$

$$L = 50 \text{ mH}$$

$$C = 1 \mu\text{F}$$

4) PSE

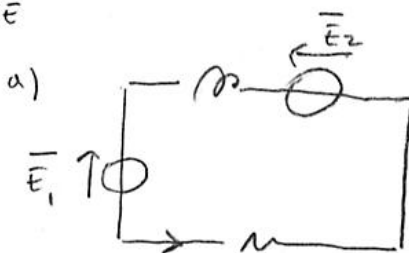

$$\bar{E}_1 = 12 e^{j45^\circ} = 12 \left(\frac{\sqrt{2}}{2} + j \frac{\sqrt{2}}{2} \right) \text{ V}$$


$$\bar{E}_2 = -j5 \text{ V}$$

$$\bar{Z}_L = j\omega L = j200$$

$$\bar{I}_a = \frac{\bar{E}_2 - \bar{E}_1}{R + \bar{Z}_L} = -0,0031 - j0,0043 = 0,0053 \angle -126^\circ$$

$$i_a(t) = R [\bar{I}_a e^{j\omega t}] = 0,0053 \cos(4000t - 126^\circ) \text{ A}$$

b)

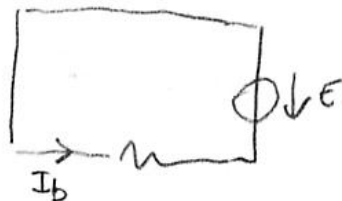

$$I_b = -\frac{E}{R} = -\frac{3}{3\text{k}} = -1 \text{ mA}$$

$$i(t) = i_a(t) + I_b = \left\{ 5,3 \cos(4000t - 126^\circ) - 1 \right\} \text{ mA}$$

1) ESPRIMERE LE SEGUENTI SOMME DI SINUSOIDI NELLA FORMA GENERALE

$$A \sin(\omega t + \phi)$$

$$- i(t) = 2 \cos(6t + 120^\circ) + 4 \sin(6t - 60^\circ) \text{ A}$$

$$- v(t) = 5\sqrt{2} \cos 8t + 10 \sin(8t + 45^\circ) \text{ V}$$

$$2) i(t) = 2 \cos(6t + 120^\circ) + 4 \sin(6t - 60^\circ) =$$

$$\bar{I} = 2 e^{j120^\circ} - j 4 e^{-j60^\circ} = 2(\cos 120^\circ + j \sin 120^\circ) - j 4(\cos 60^\circ - j \sin 60^\circ)$$

$$= 2\left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) - j 4\left(\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \text{ A}$$

$$= -1 + j\sqrt{3} - 2\sqrt{3} - j 2 = -4,464 - j 0,268$$

$$= 4,472 \angle -176,565^\circ \text{ A}$$

$$i(t) = 4,472 \cos(6t - 176,565^\circ) = 4,472 \sin(6t + 93,435^\circ) \text{ A}$$

$$v(t) = 5\sqrt{2} \cos 8t + 10 \sin(8t + 45^\circ) =$$

$$\bar{V} = 5\sqrt{2} - j 10 e^{j45^\circ} = 5\sqrt{2} - j 10(\cos 45^\circ + j \sin 45^\circ)$$


$$= 5\sqrt{2} - j 10\left(\frac{\sqrt{2}}{2} + j\frac{\sqrt{2}}{2}\right) \text{ V}$$

$$= 5\sqrt{2} - j 5\sqrt{2} + 5\sqrt{2} = 14,142 - j 7,071$$

$$= 15,811 \angle -26,565^\circ \text{ V}$$

$$v(t) = 15,811 \cos(8t - 26,565^\circ) = 15,811 \sin(8t - 116,565^\circ) \text{ V}$$

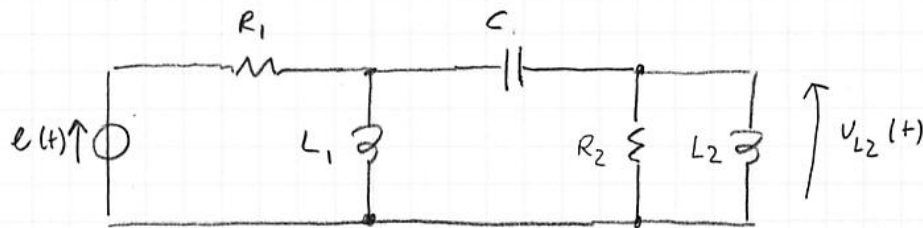
2) DETERMINARE $e(t)$ SAPENDO CHE $v_{L2}(t) = 10 \cos 400t$ V



$$\begin{aligned} R_1 &= 25 \Omega \\ L_1 &= 0,06 \text{ H} \\ C &= 80 \mu\text{F} \\ R_2 &= 40 \Omega \\ L_2 &= 0,15 \text{ H} \end{aligned}$$

$$\begin{aligned} 2) \quad \bar{V}_{L2} &= 10 \text{ V} \quad \bar{Z}_{L1} = j\omega L_1 = j400 \cdot 0,06 \Omega = j24 \Omega \quad \bar{Z}_{L2} = j\omega L_2 = j400 \cdot 0,15 \Omega = j60 \Omega \quad \bar{Z}_C = -j\frac{1}{\omega C} = -j\frac{1}{400 \cdot 80 \cdot 10^{-6}} \Omega = -j31,25 \Omega \\ \bar{I}_{R2} &= \frac{\bar{V}_{L2}}{R_2} = \frac{10}{40} = 0,25 \text{ A} \\ \bar{I}_{L2} &= \frac{\bar{V}_{L2}}{\bar{Z}_{L2}} = -j0,16 \text{ A} \\ \bar{I}_C &= \bar{I}_{R2} + \bar{I}_{L2} = 0,25 - j0,16 \text{ A} \\ \bar{V}_C &= \bar{Z}_C \cdot \bar{I}_C = -5,208 - j7,813 \text{ V} \\ \bar{V}_{L1} &= \bar{V}_C + \bar{V}_{L2} = 4,792 - j7,813 \text{ V} \\ \bar{I}_{L1} &= \frac{\bar{V}_{L1}}{\bar{Z}_{L1}} = -0,326 - j0,2 \text{ A} \\ \bar{I}_{R1} &= \bar{I}_C + \bar{I}_{L1} = -0,076 - j0,366 \text{ A} \\ \bar{V}_{R1} &= R_1 \bar{I}_{R1} = -1,89 - j9,158 \text{ V} \\ \bar{E} &= \bar{V}_{R1} + \bar{V}_{L1} = 2,904 - j16,971 \text{ V} = 17,218 \angle -80,29^\circ \text{ V} \\ e(t) &= \Re[\bar{E} e^{j\omega t}] = 17,218 \cos(400t - 80,29^\circ) \text{ V} \end{aligned}$$

3) DETERMINE $i(t)$

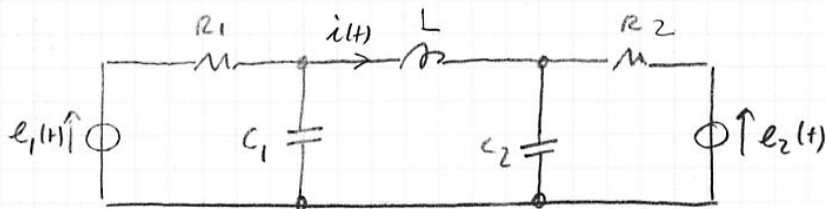

$$\begin{aligned} e_1(t) &= 10 \cos \omega t \text{ V} \\ e_2(t) &= 10 \sin \omega t \text{ V} \\ \omega &= 1000 \text{ rad/s} \\ R_1 &= 10 \Omega \quad R_2 = 1 \Omega \\ C_1 &= C_2 = 1 \text{ mF} \quad L = 1 \text{ mH} \end{aligned}$$


3) $\bar{E}_1 = 10 \text{ V} \quad \bar{E}_2 = -j10 \text{ V}$
 $\bar{Z}_{C1} = \bar{Z}_{C2} = -j \frac{1}{\omega C} = -j \frac{1}{1000 \cdot 10^{-3}} = -j1 \Omega \quad \bar{Z}_L = j\omega L = j10^3 \cdot 10^{-3} = j1 \Omega$

$$\bar{A}_1 = \frac{\bar{E}_1}{R_1} = 1 \text{ A}$$

$$\bar{A}_2 = \frac{\bar{E}_2}{R_2} = -j10 \text{ A}$$


$$\bar{Z}_1 = R_1 \parallel \bar{Z}_{C1} = (R_1^{-1} + \bar{Z}_{C1}^{-1})^{-1} = 0,099 - j0,99 \Omega$$
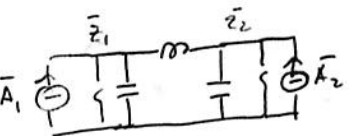
$$\bar{Z}_2 = R_2 \parallel \bar{Z}_{C2} = (R_2^{-1} + \bar{Z}_{C2}^{-1})^{-1} = 0,5 - j0,5 \Omega$$



$$\bar{E}_{A1} = \frac{\bar{E}_1}{R_1}, \bar{Z}_1 = 0,099 - j0,99 \Omega$$

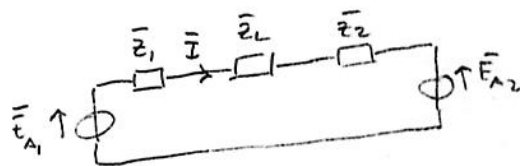
$$\bar{E}_{A2} = \frac{\bar{E}_2}{R_2}, \bar{Z}_2 = -0,5 - j0,5 \Omega$$



$$\bar{I} = \frac{\bar{E}_{A1} - \bar{E}_{A2}}{\bar{Z}_1 + \bar{Z}_L + \bar{Z}_2} = \frac{5,099 - j4,010}{0,099 - j0,99 + j1 + 0,5 - j0,5} = 1,819 + j8,182 = 8,382 \angle 77,466^\circ \text{ A}$$

$$i(t) = R[\bar{I} e^{j\omega t}] = 8,382 \cos(1000t + 77,466^\circ) \text{ A}$$

4) DETERMINE $i(t)$

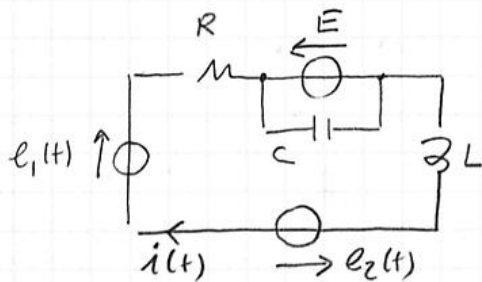

$$e_1(t) = 12 \cos(4t + 45^\circ) \text{ V}$$

$$e_2(t) = 5 \sin 4t \text{ V}$$



$$E = 3 \text{ V}$$

$$R = 6 \text{ k}\Omega$$

$$L = 0,5 \text{ H}$$

$$C = 100 \mu\text{F}$$

4) PSE

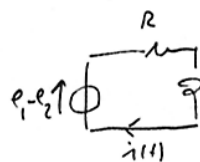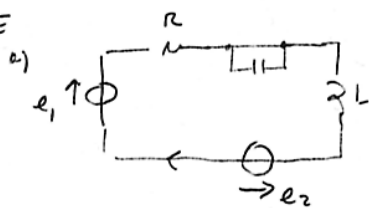


$$\bar{E}_1 - \bar{E}_2 = 12e^{j45^\circ} = 8,485 + j13,485 \text{ V}$$

$$\bar{I} = \frac{\bar{E}_1 - \bar{E}_2}{R + j\omega L} = \frac{12e^{j45^\circ}}{6 \cdot 10^3 + j2} = 1,415 + j2,247 \text{ mA}$$

$$= 2,655 \angle 57,86^\circ \text{ mA}$$
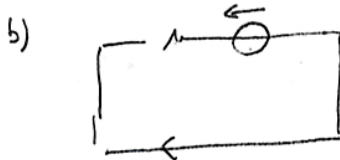
$$i_a = R[\bar{I}e^{j\omega t}] = I_a \cos(4t + \phi_I) = 2,655 \cos(4t + 57,80^\circ) \text{ mA}$$



$$I_b = -\frac{E}{R} = -\frac{3}{6 \text{ k}\Omega} = -0,5 \text{ mA}$$

$$i_r = i_a + i_b = \{2,655 \cos(4t + 57,80^\circ) - 0,5\} \text{ mA}$$